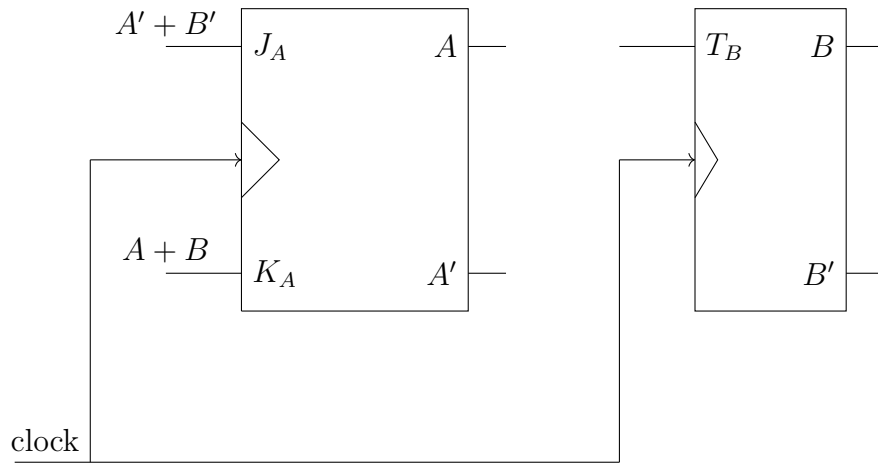


# Assignment

January 9, 2024

## Gate Question

1. Given below is the diagram of a synchronous sequential circuit with one  $J - K$  flip-flop and one  $T$  flip-flop with their outputs denoted as  $A$  and  $B$  respectively, with  $J_A = (A' + B')$ ,  $K_A = (A + B)$  and  $T_B = A$ .



Starting from the initial state ( $AB = 00$ ), the sequence of states ( $AB$ ) visited by the circuit is

- (a)  $00 \rightarrow 01 \rightarrow 10 \rightarrow 11 \rightarrow 00 \dots$
- (b)  $00 \rightarrow 10 \rightarrow 01 \rightarrow 11 \rightarrow 00 \dots$
- (c)  $00 \rightarrow 10 \rightarrow 11 \rightarrow 01 \rightarrow 00 \dots$
- (d)  $00 \rightarrow 01 \rightarrow 11 \rightarrow 00 \dots$